

## **EXPERIMENT -8**

### **RC PHASE SHIFT OSCILLATOR**

**AIM:** To design a RC Phase Shift Oscillator with following specifications and to verify the phase shift ( $180^\circ$ ) and find the frequency of oscillations.

#### **DESIGN SPECIFICATIONS:**

$V_{cc} = 12V$ ,  $R_1 = 18.3k$ ,  $R_2 = 6.8k$ ,  $R_e = 1k$ ,  $R_c = 2.2k$ ,  $C_1 = C_2 = C_3 = 0.1\mu F$ ,  $R_1 = R_2 = 4.7K\Omega$ ,  $R_3 = 3.3K\Omega$ , NPN transistor with  $\beta$  value 100.

#### **APPARATUS:**

- CRO
- Regulated DC power supply
- Decade resistance Box
- Decade capacitance Box
- Decade inductance Box
- Resistors
- Capacitors
- Transistor
- Bread board, Single strand wires


#### **SOFTWARE SIMULATION:**

**Software used:** Multisim Analog Devices Edition 14.0

#### **Procedure:**

1. Switch ON the computer and open the Multisim software
2. Observe Design tool box, Instrumentation tool box, component tool box and its component functionality
3. From above tool boxes, Connect the circuit using the designed values of each and every component
4. Connect the output of amplifier to input of  $\beta$ -network[RC Combination] and output of  $\beta$ -network to input of amplifier.
5. Connect the Cathode Ray Oscilloscope (CRO) to the input and output terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO observe the following values:
  - Frequency of Oscillations
  - Phase Shift =  $180^\circ$

## **SIMULATION OF THE DESIGN:**

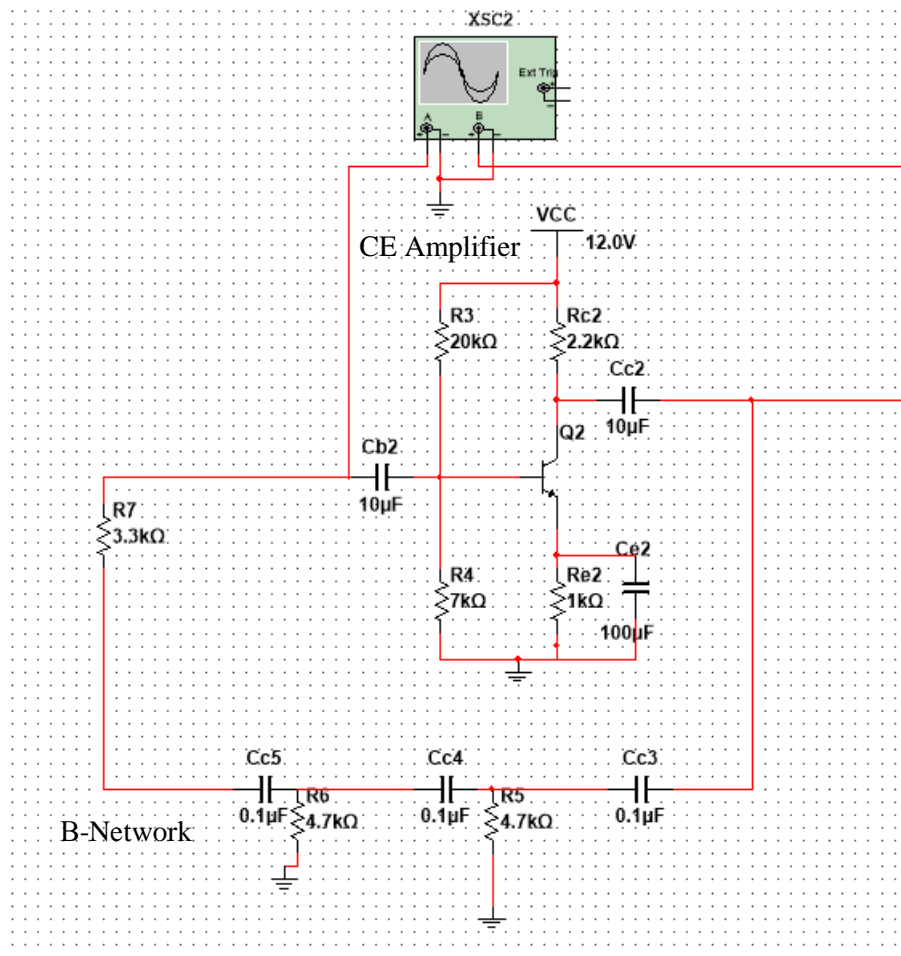

RC Phase Shift Oscillator circuit

## **❖ OBSERVATIONS:**

### **Phase Shift:**



## **Conclusion:**

From the above waveform we can conclude that the overall phase shift b/w input and output signal is 180°.

## HARDWARE SIMULATION:

### Procedure:

1. Connect the circuit as per the circuit diagram.
2. Apply the supply voltage,  $V_{cc}=12V$
3. Make sure that the transistor is operating point in active region by keeping  $V_{CE}$  half of  $V_{CC}$ .
4. Now note down the phase shift b/w different O/P Terminals.
5. Now calculate the theoretical frequency of oscillations generated.

### Observations:

Colpitt's Oscillator

Probe Location	Phase Shift
Cc3	
Cc4	
Cc5	

**Conclusion:** Ideally for individual RC Beta Network the phase shift offered by them should be  $60^\circ$  but in practical they offer approximately equal to  $60^\circ$  but in overall phase shift offered by the 3 RC networks is  $180^\circ$ .