

## **EXPERIMENT -4** **DARLINGTON AMPLIFIER**

**AIM:** To design a Darlington amplifier with following specifications and to verify the gain at different stages.

### **DESIGN SPECIFICATIONS:**

$V_{cc} = 12V$ ,  $R_1 = 1M$ ,  $R_2 = 1.5M$ ,  $R_e = 2.2k$ , NPN transistor with  $\beta$  value 100.

### **SOFTWARE SIMULATION:**

**Software used:** Multisim Analog Devices Edition 14.0

### **Procedure:**

1. Switch ON the computer and open the Multisim software
2. Observe Design tool box, Instrumentation tool box, component tool box and its component functionality
3. From above tool boxes, Connect the circuit using the designed values of each and every component
4. Connect the function generator with sine wave of 6v p-p as input at the input terminals of the circuit. (Or) use signal source.
5. Connect the Cathode Ray Oscilloscope (CRO) to the output terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO observe the following values:
  - Input voltage  $V_i$
  - Output voltage  $V_o$
  - Voltage Gain  $A_v = 1$
  - Current Gain  $A_i = \text{Max} = 100 \times 100$
  - Phase Shift  $= 0^\circ$
8. Calculate the input impedance of the circuit and prove input impedance of Darlington pair is greater than CC Amplifier.

**Design Calculations:**

Given Data:

$$I_c = 2.5\text{mA}$$

$$\beta = 100$$

$$V_{cc} = 12\text{V}$$

**Calculation of  $R_e$ :**

$$Q\text{Point}(V_{ce}, I_c) = (6\text{V}, 2.5\text{mA})$$

$$R_e = V_{ce} / I_c = 6\text{V} / 2.5\text{mA} = 2.4\text{k}\Omega$$

**Calculation of  $R_1$  and  $R_2$ :**

$$\text{Voltage acting at base} = (6 + 0.7 + 0.7) \text{ V}$$

By Applying Voltage division,

$$12 * R_2 / (R_1 + R_2) = 7.4$$

$$R_1 = 0.639 R_2$$

We know that,

$$R_2 < \beta^2 * 2.4\text{k}\Omega \quad R_2 < 10000 * 2.4\text{k}\Omega$$

$$R_2 < 24\text{M}\Omega$$

$$R_2 = 1.5\text{M}\Omega$$

$$R_1 = 1\text{M}\Omega$$


**THEORETICAL CALCULATION OF INPUT RESISTANCE:**

$$R_s = R_1 \parallel R_2 \parallel \beta^2 R_e$$

$$R_s = (1\text{M} \parallel 1.5\text{M} \parallel 10000 * 2.4\text{K}) \Omega$$

$$R_s = 600\text{K} \Omega$$


## SIMULATION OF THE DESIGN:

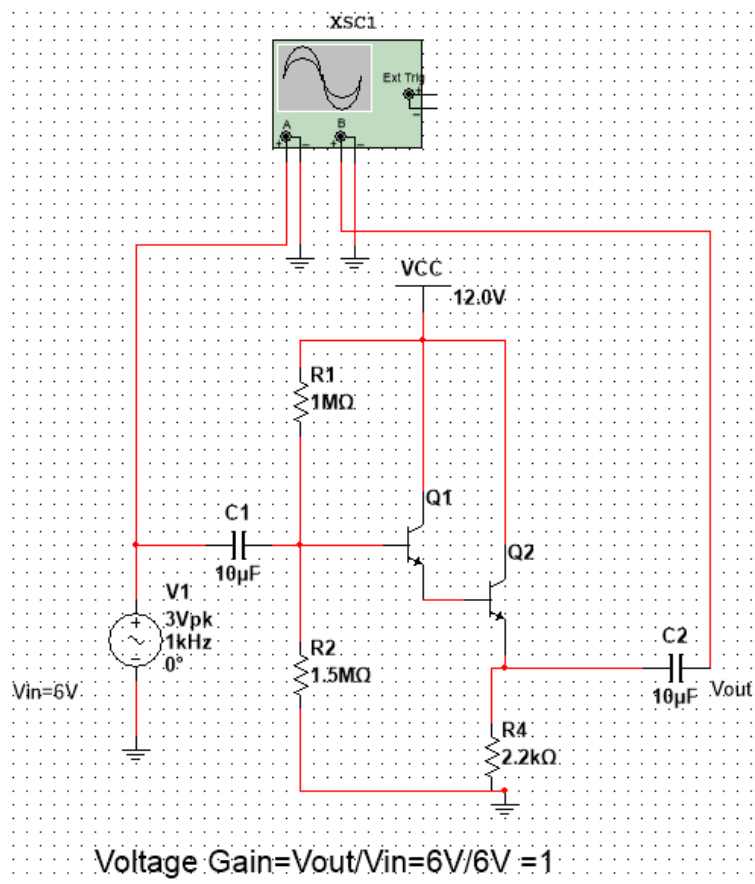

Darlington Amplifier circuit

## ❖ OBSERVATIONS:


### Voltage Gain:

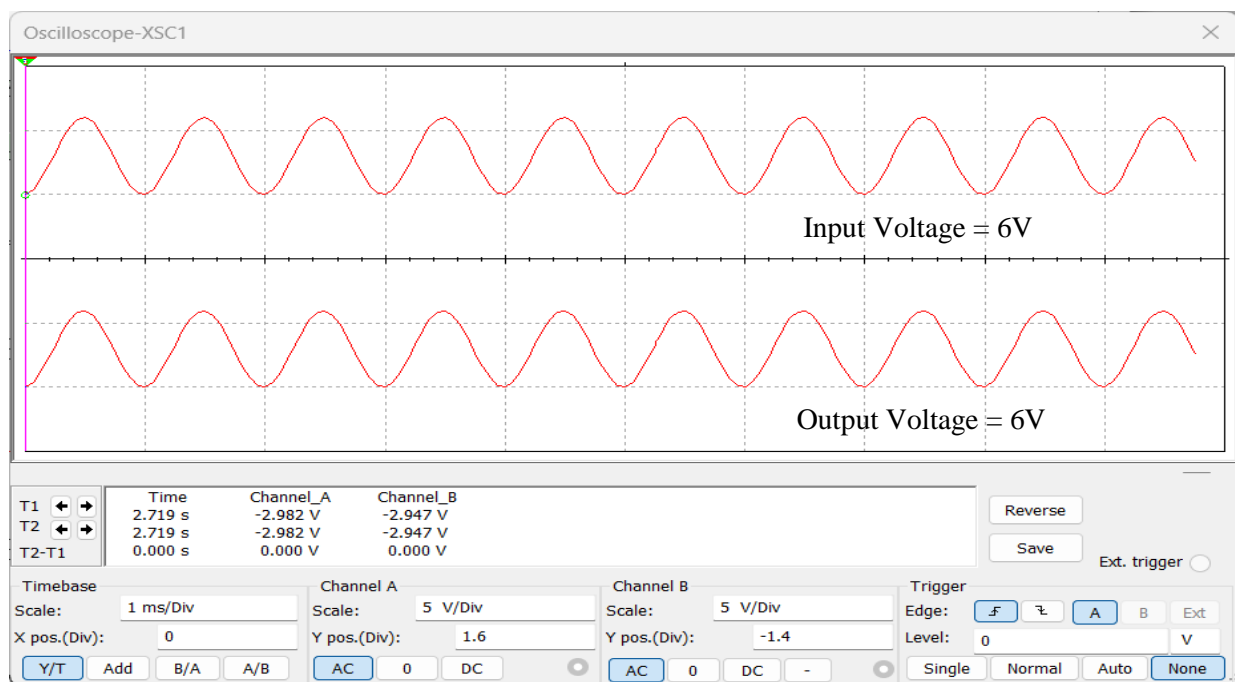

## **Conclusion:**

Voltage Gain of Darlington Amplifier is 1.

## Current Gain:

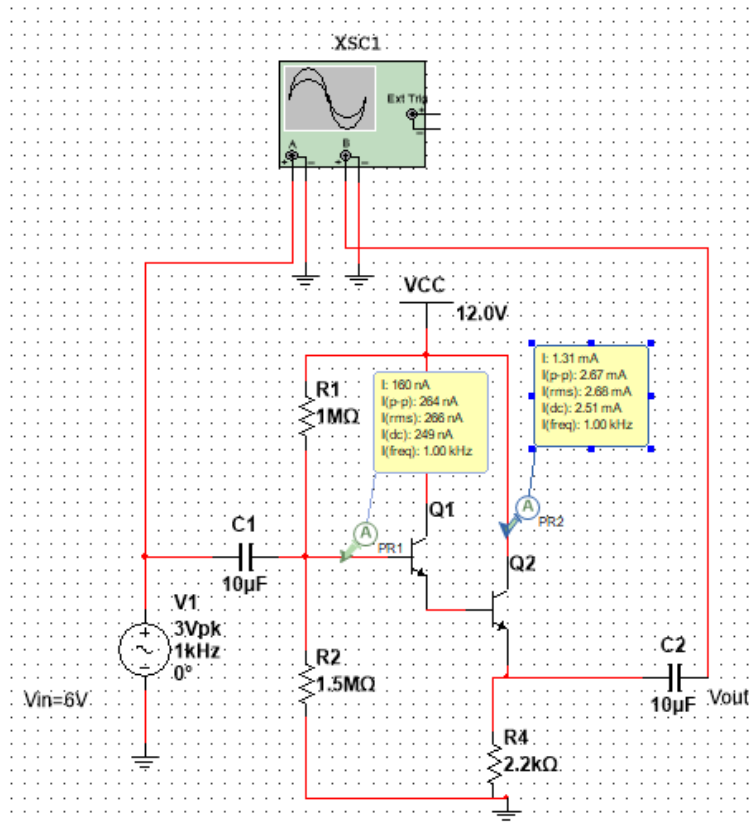

## Conclusion:


$$I_{in} = 264 nA$$

$$I_{out} = 267 mA$$

$$A_i = I_{out} / I_{in} \\ = 267 mA / 264 nA$$


$$A_i = 10000 = 100 * 100 \\ = h_{fe} * h_{fe}$$

## Phase Shift:

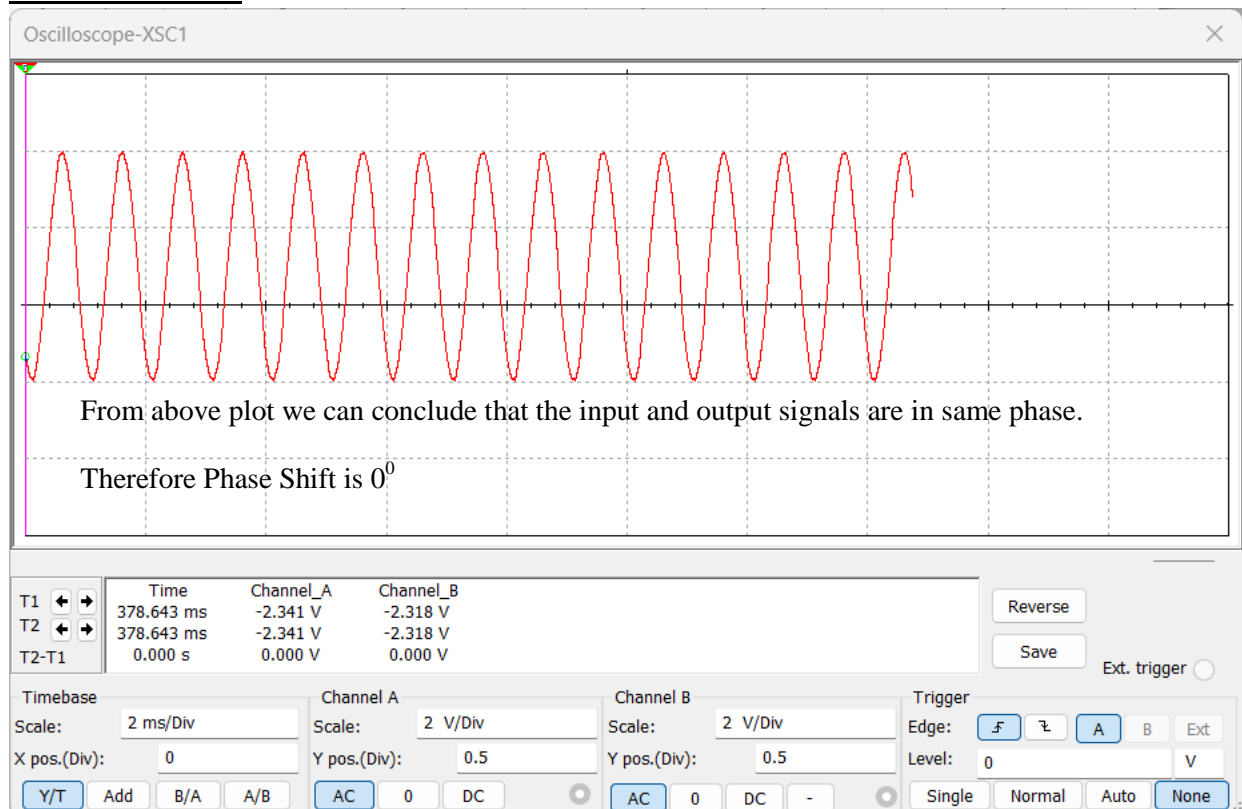


## PRACTICAL CALCULATION OF INPUT RESISTANCE:

### Case 1: $R_{in}=100k\Omega$

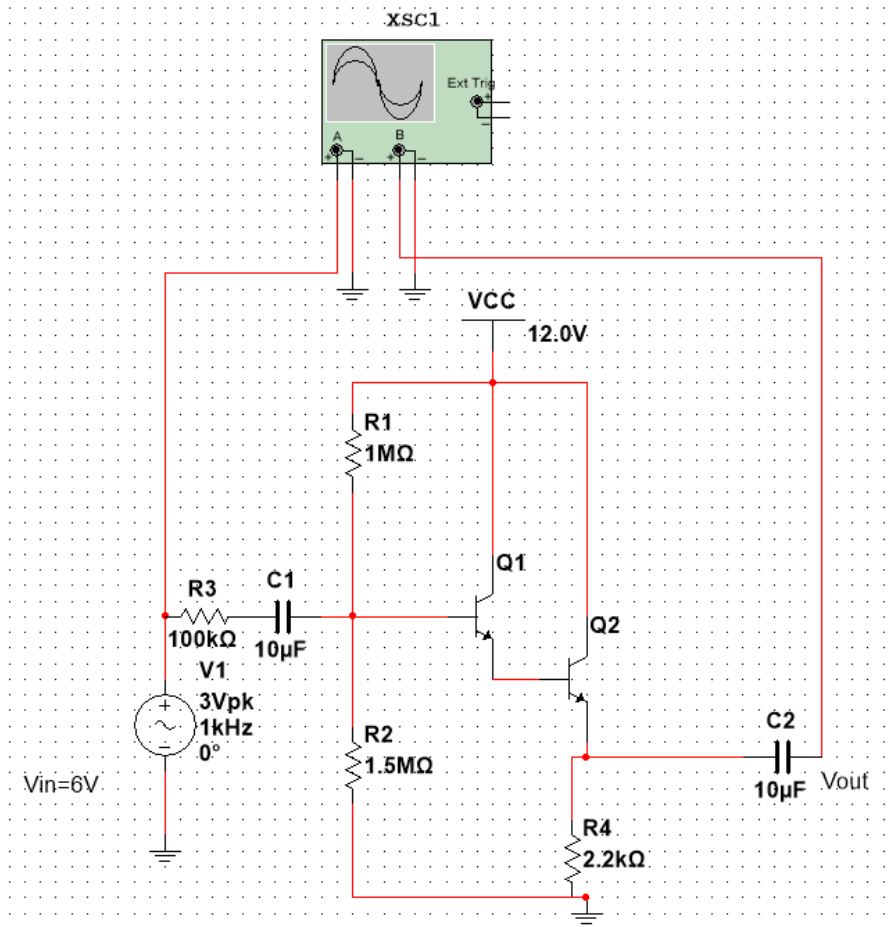


### OUTPUT:

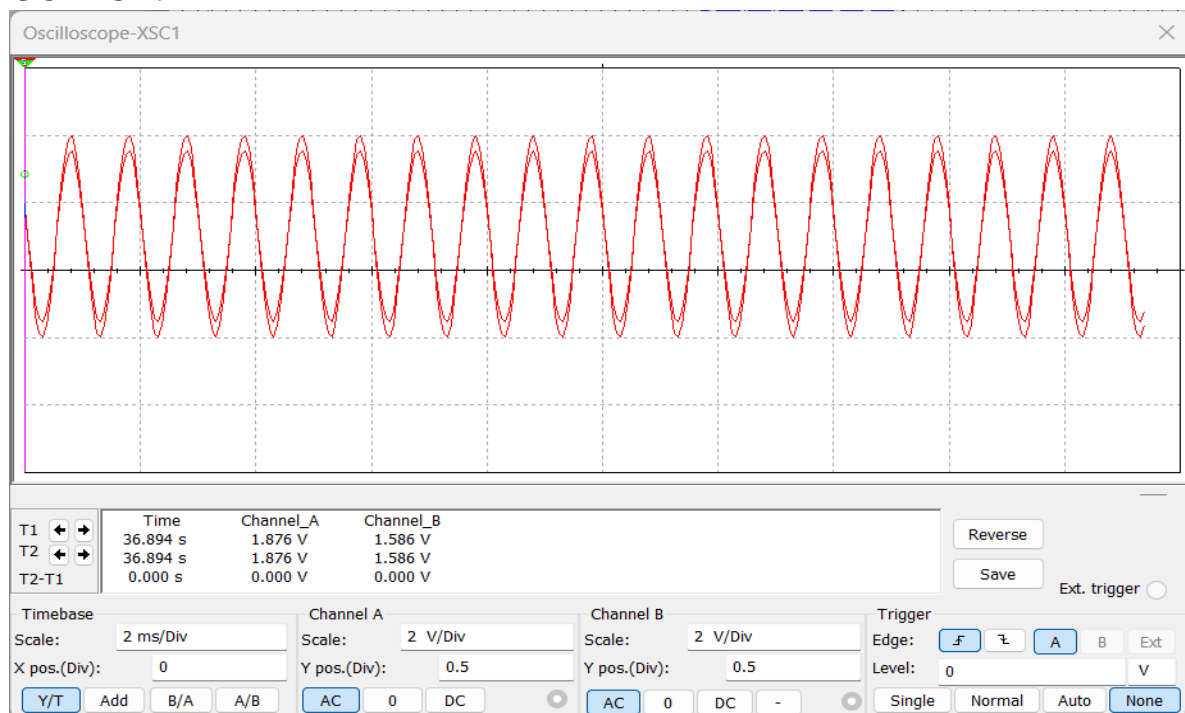


### Conclusion:

After introducing source resistance  $R_s$  the input voltage decreased.

## Case 2: $R_{in}=584k\Omega$

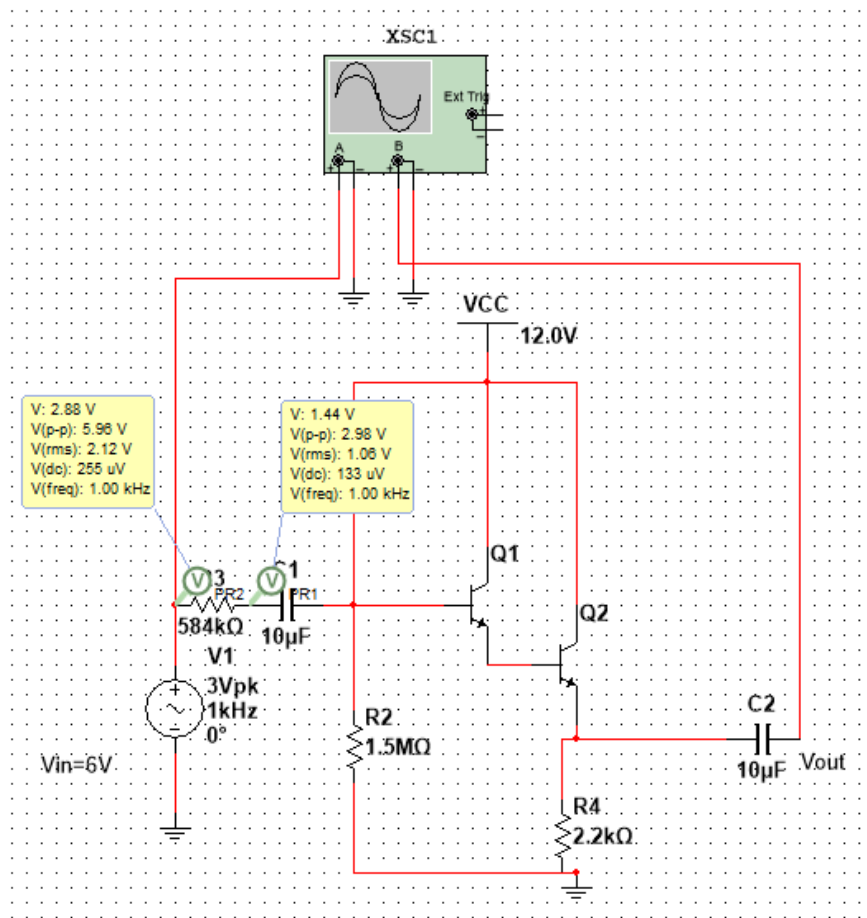

## OUTPUT:

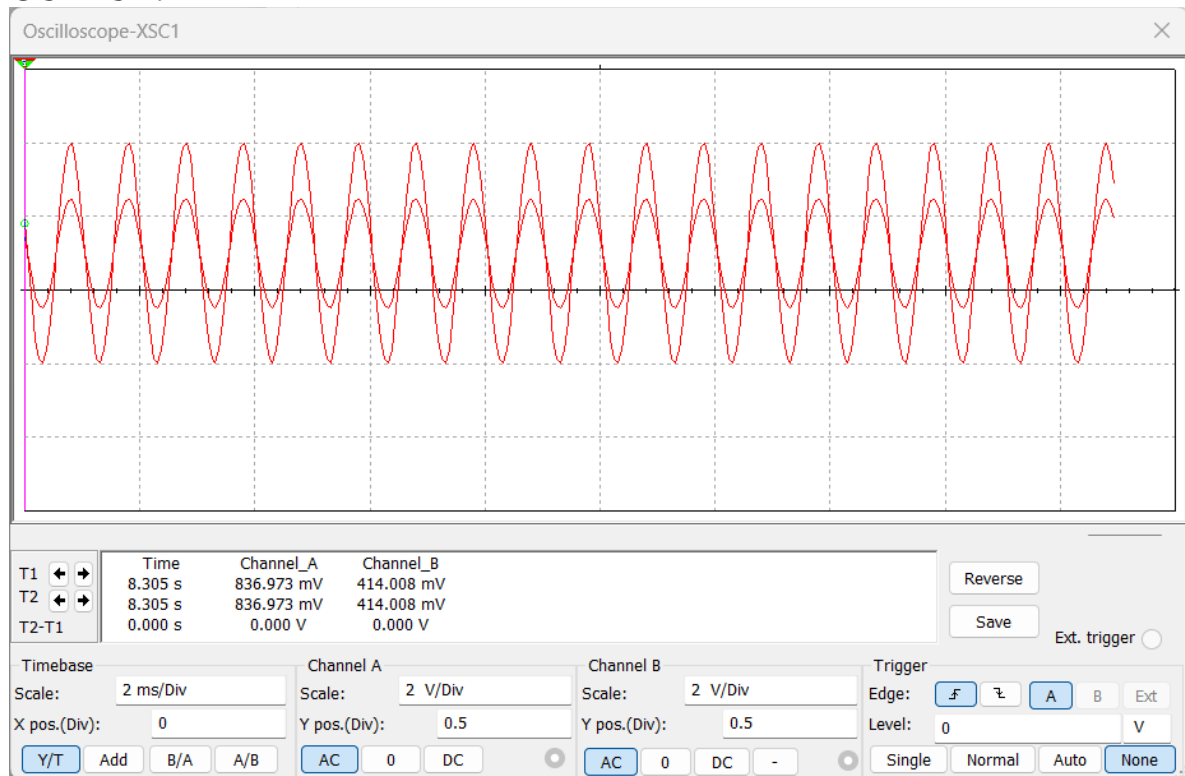


## Observation:

Output is half of the input, therefore the input resistance of the amplifier is equal to the added source resistance i.e., 584k and input resistance of Darlington

Amplifier is much greater than Single CC Amplifier i.e,  $10k\Omega$ .

### **FREQUENCY RESPONSE:**

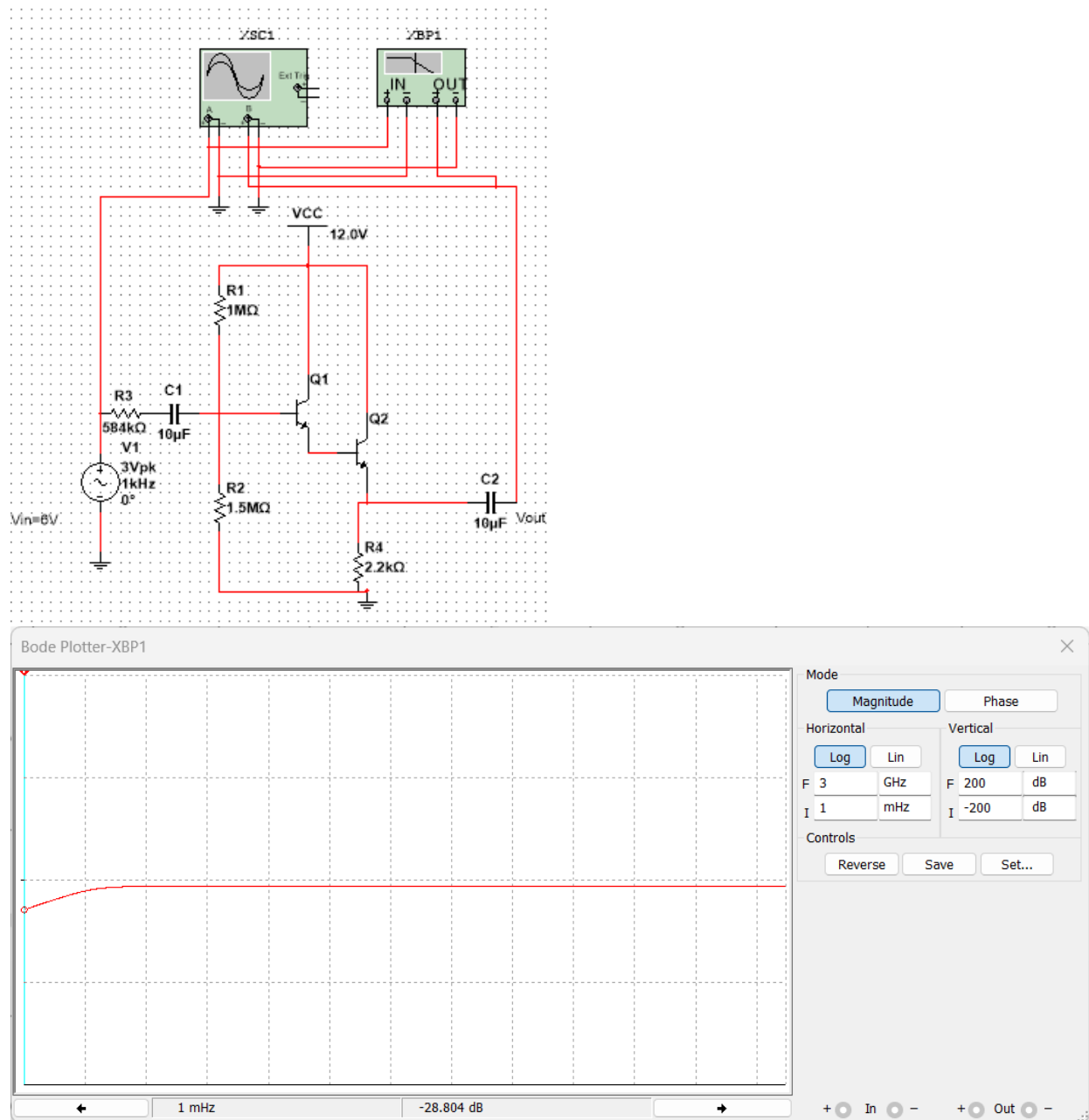

### **CONCLUSION:**

From the above observations, we can conclude that in a Darlington Amplifier:

Voltage Gain: 1

Current Gain:  $h_{fe} \times h_{fe} = 100 \times 100$

$R_{in}$ :  $584K \Omega$